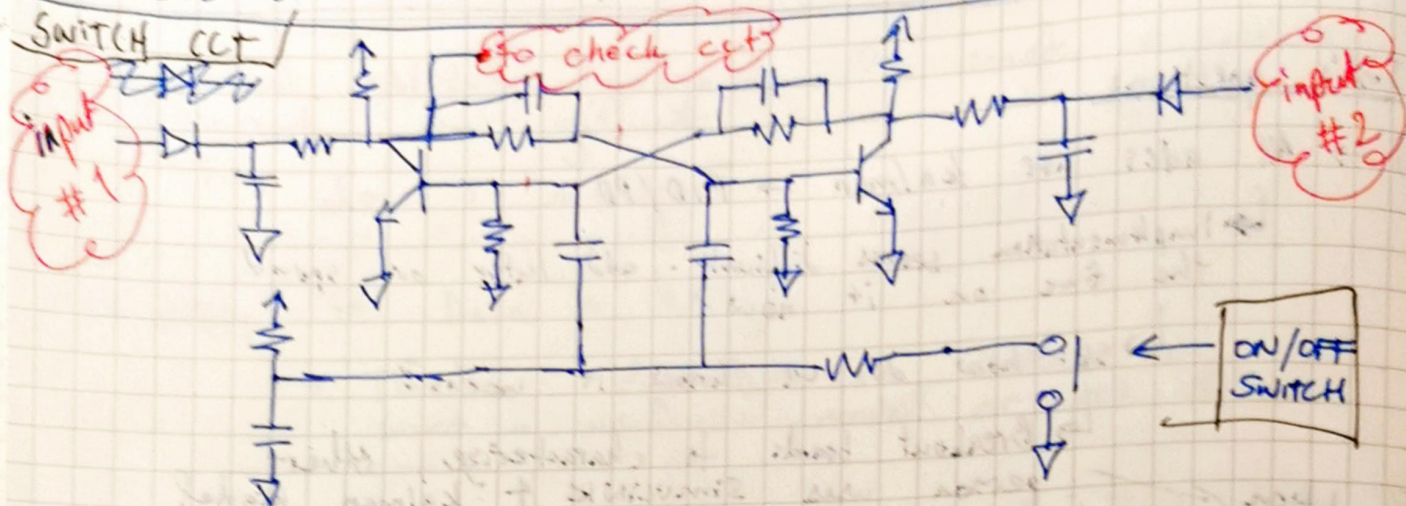


HACKED 2021


2021-01-16

SWITCH CCT




OUTPUT BUFFER

from GE-7

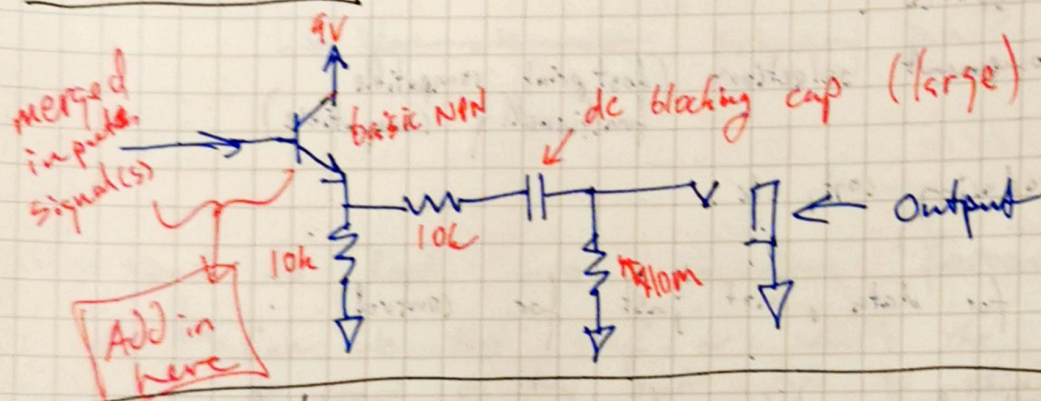


input polarity

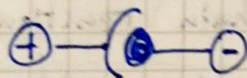


(bass reverse std)


Block diagram

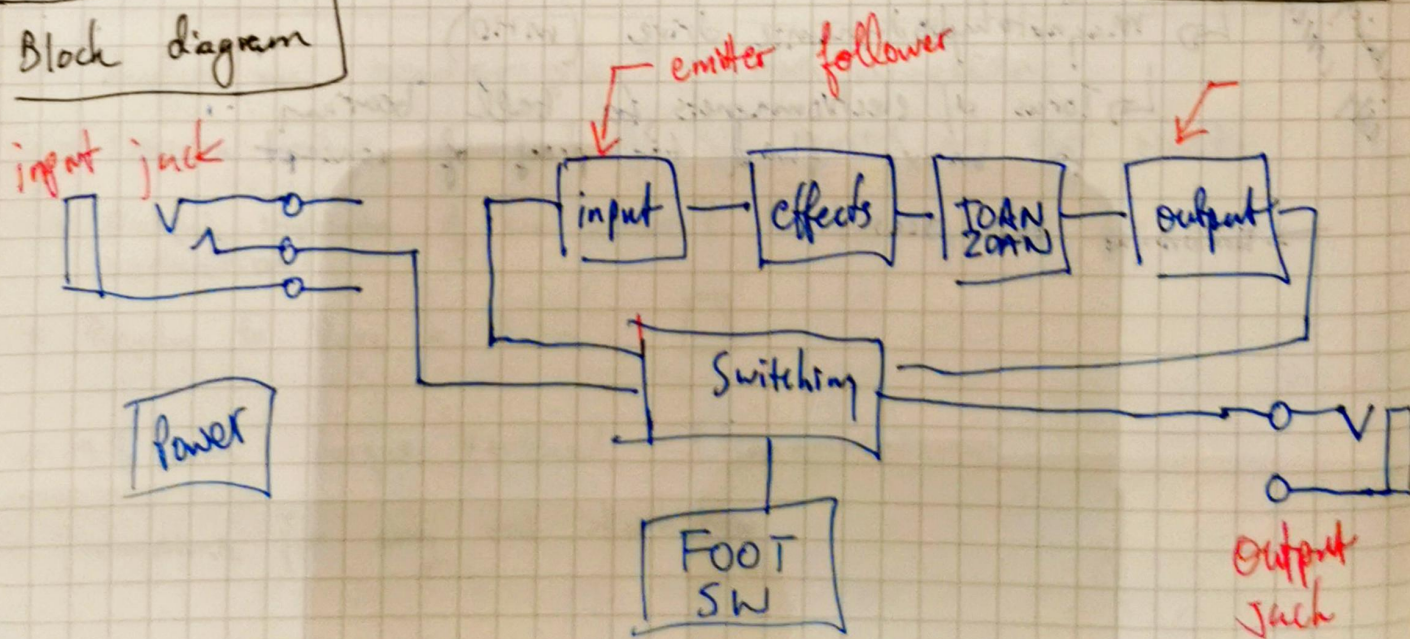


input buffer sch

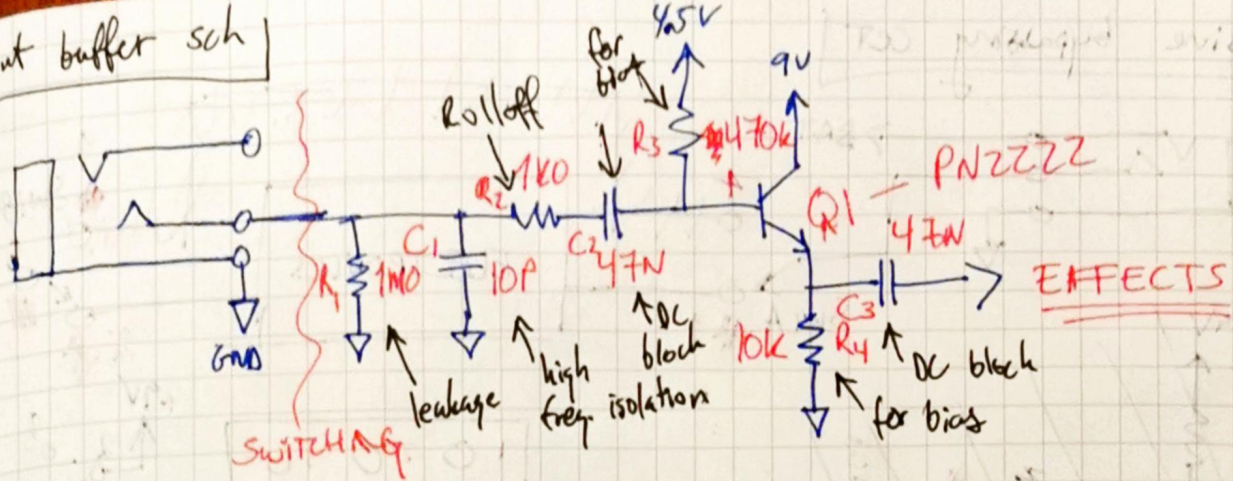


output buffer #2

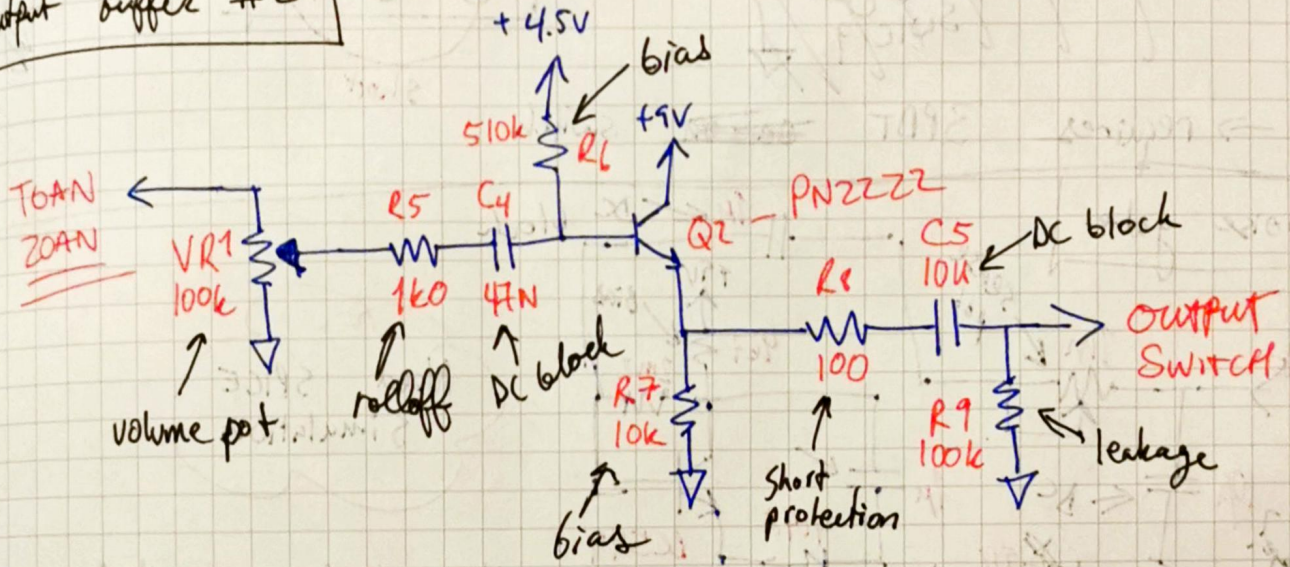

Power CCT

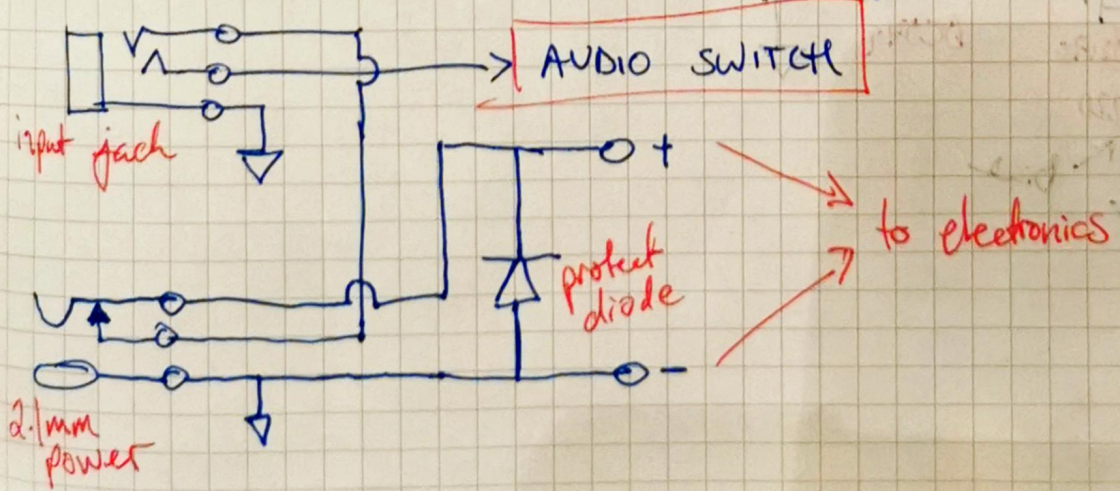


Passive bypassing CCT

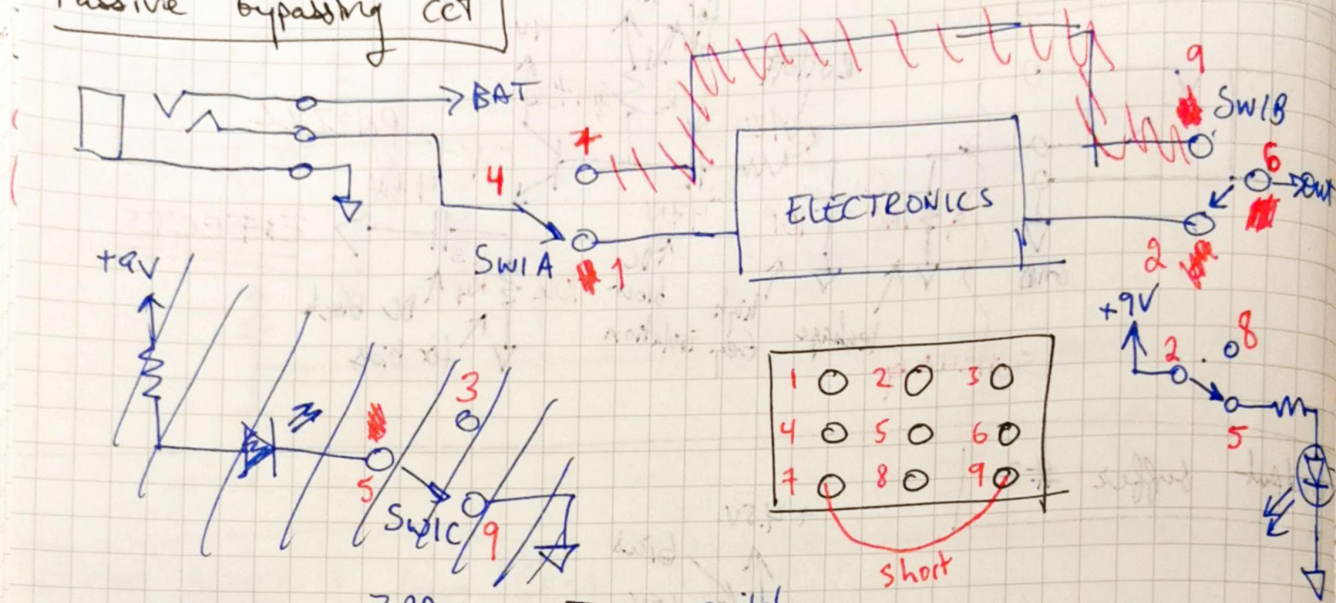

→ requires 3PDT ~~on-on~~ switch


Noise gate

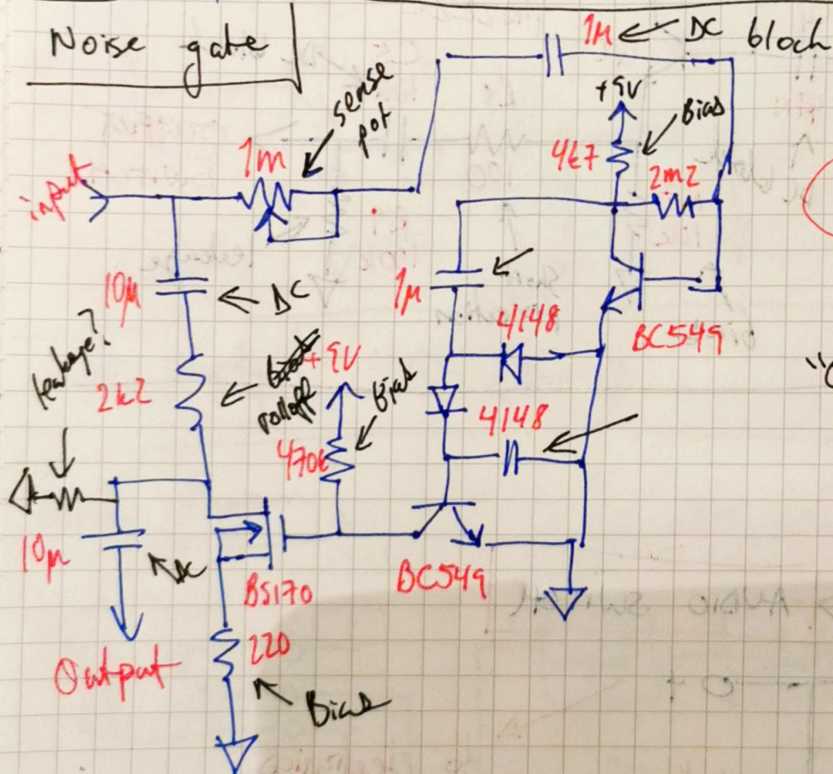

Need SPICE simulation

"One knob noise gate"

Basic Equalizer for Bass/mid/Treb.

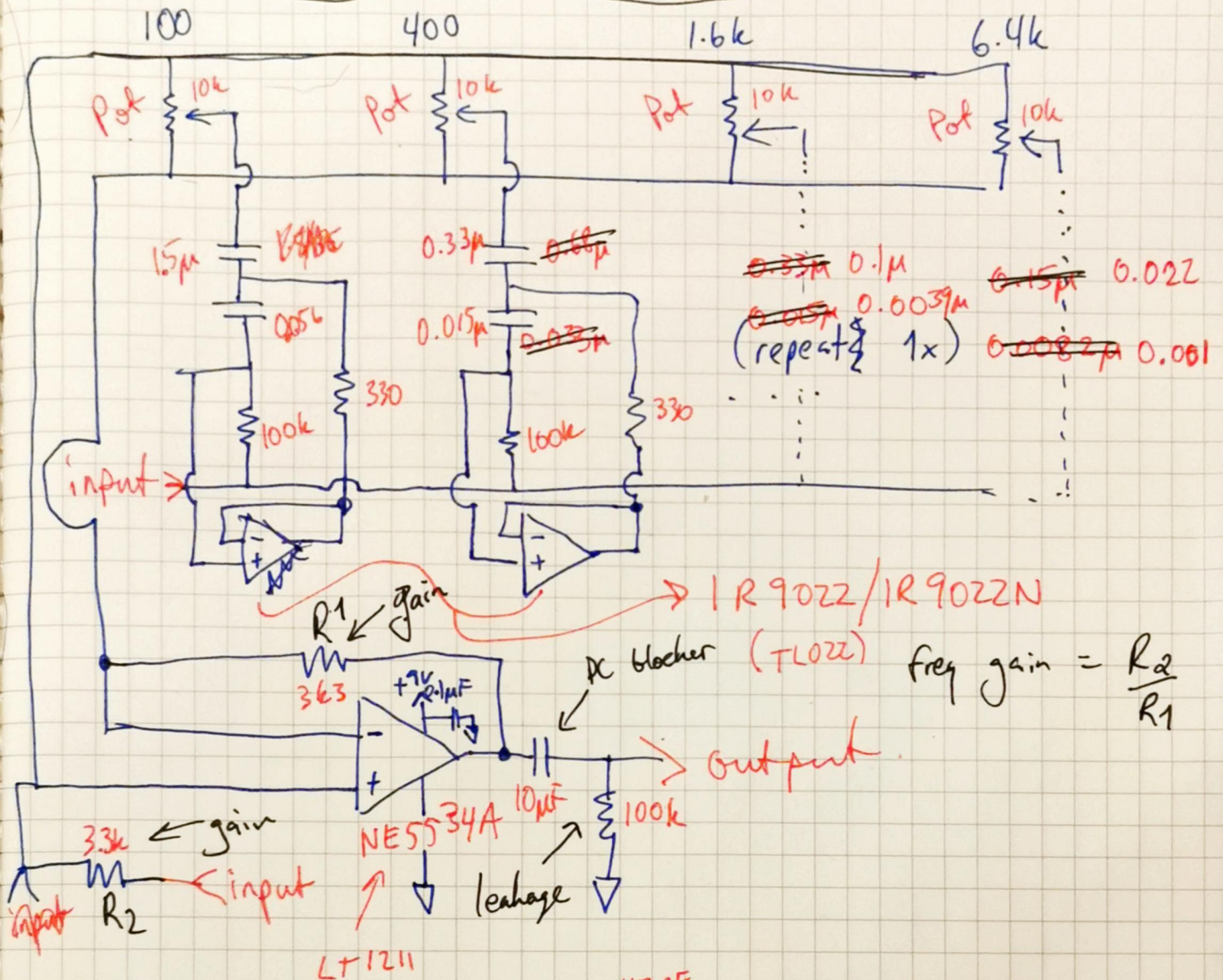

Distortion Stage

